

# Digital System Design Applications

## Final Project Report

(Project Number 4)

Hasan Enes Şimşek

040160221

08.02.2021

## 1. About the Project

Using one of the methods described at [3], calculate  $C = \frac{A}{B}$  where A is a 8-bit positive integer and B is a 4-bit positive integer. There will be two 8-bit positive integer outputs as quotient,  $Q$ , and remainder,  $R$ .

According to the reference given in the project instruction above, I used the algorithm as seen in the [1, Fig. 1] where N is dividend, D is divider, Q is quotient, R is remainder. I will increase quotient +1 every time I subtract divider from dividend. In the final, last result of the subtraction will be remainder and iteration number will be quotient as I increase every iterations.

```
function divide_unsigned(N, D)
  Q := 0; R := N
  while R ≥ D do
    Q := Q + 1
    R := R - D
  end
  return (Q, R)
end
```

**Figure 1:** A Division Algorithm for Unsigned Binary Numbers.

## 2. Pseudo Code of the algorithm

Before explaining Algorithmic State Machine design, it is good to produce pseudo code that is more abstract than ASM.

```
Get N to reg15
reg 14 = 0 //reset Q
Get_Divider:
  Get D to reg1
  Reg1<<1
  if Z=1,
    reg0 = 0 // Control "divide by zero" condition
  Load 1111_1111 to reg2
  Reg2 = reg2 + reg1
  Load 0000_0001 to reg1
  Reg2 = reg2 + reg1
  Move reg15 to reg1
  Calculate reg1+reg2
  If C=1,
    reg15 = reg1
    Goto cont: //continue subtraction
  Else If C=0,
    reg1 = reg15
```

```


Goto stop: //stop process
Stop:
  Reg0 = reg14
Cont:
  Reg1 = reg14
  Load 0000_0001 to reg2
  Reg14 = reg1 + reg2
  Goto Get_Divider

```

**Code 1:** Pseudo Code of the CU

I will explain details in ASM.

### 3. Algorithmic State Machine

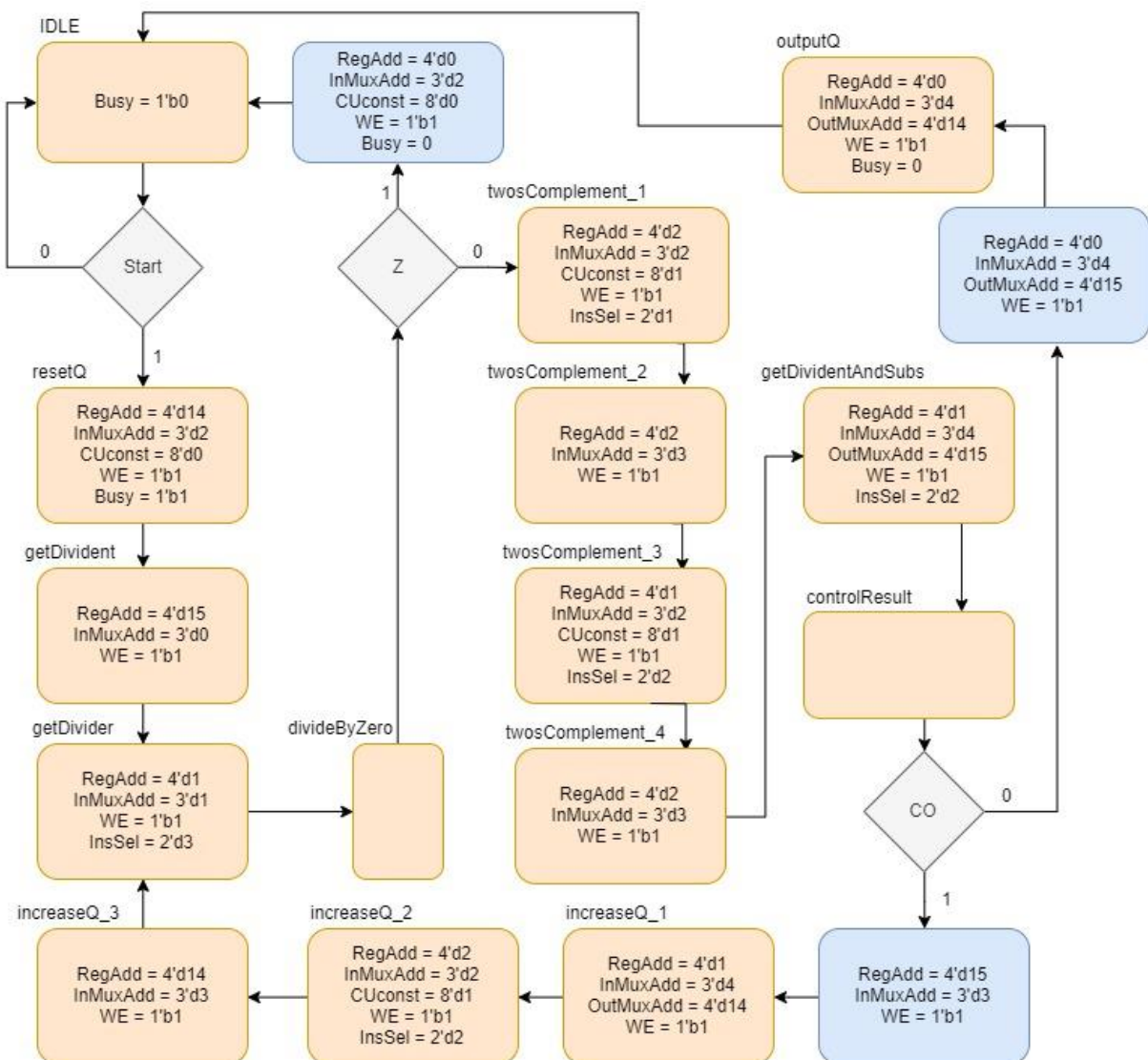

**Figure 2:** ASM of the Designed CU

In the **IDLE** state, circuit is ready to get inputs and start signal to operate.

After getting **Start** signal, circuit goes **resetQ** state.

In the **resetQ** state, Q(quotient) is set to zero. Register14 is reserved for Q.

The, with **getDivident** state, dividend is taken as external input from **inA**. Register15 is reserved for remainder. In the final, this register becomes remainder instead of dividend.

Like dividend, divider is taken as external input from **inB** in the state **getDivider**. And circular left shift operation is done with divider.

If the **Z flag** is 1, then ASM goes idle state while producing output zero. (zero divider error)

If the **Z flag** is 0, then ASM goes twosComplement\_1 state.

In the **twosComplement\_1, \_2, \_3 and \_4 states**, I am calculating  $N = N - D$  operation. However, designed ALU has only adder circuit, so firstly I need to find two's complement of D and I should sum with N.

More specifically, in the state **twosComplement\_1**, NOT D operation is done. However, there is no NOT gate in the ALU, so (D XOR 1111\_1111) is used instead.

In the **twosComplement\_2**, output of the operation coming from ALU, is written into register 2.

In the **twosComplement\_3**, calculated NOT D is summed with number 1 to get two's complement of D. (two's comp of D = NOT D +1)

In the **twosComplement\_4**, output of the operation coming from ALU, is written into register 2.

In the **getDividentAndSubs**,  $N = N - D$  operation is calculated as summing N and two's comp. of D. Firstly N is getting from reserved register15 to reg1 and summed with  $-D$  in the reigister1.

In the **controlResult**, if **CO flag is 1**, calculation is continue with increaseQ registers(**N=>D**). Output of the sum is written into reg 15.

- **increaseQ\_1 state:** previous Q in the reserved register 14 is written into reg1
- **increaseQ\_2 state:** previous Q is summed with 1
- **increaseQ\_3 state:** increased Q is written into reserved register14. Next state is getDivider. So calculation is continuing. Circuit will calculate  $N = N - D$  again.


If **CO flag is 0**( $N < D$ ), calculation is done. Output is not written. Previous output is written into reg1 in order to generate external output. Thanks to this state, **remainder stays 1 clock cycle in the output port**. Then it goes to **outputQ** state.

- In the **outputQ** state, register 14 is written into register1 to generate **quotient** in output. Next state is idle state so output stays until new start signal has come.

Note: In the project instructions, dividend is set as 8-bit unsigned, divisor is set as 4-bit unsigned integer. I use 4-bit zero padding for divisor.

## 4. RTL Schematics

### 4.1 Top Module

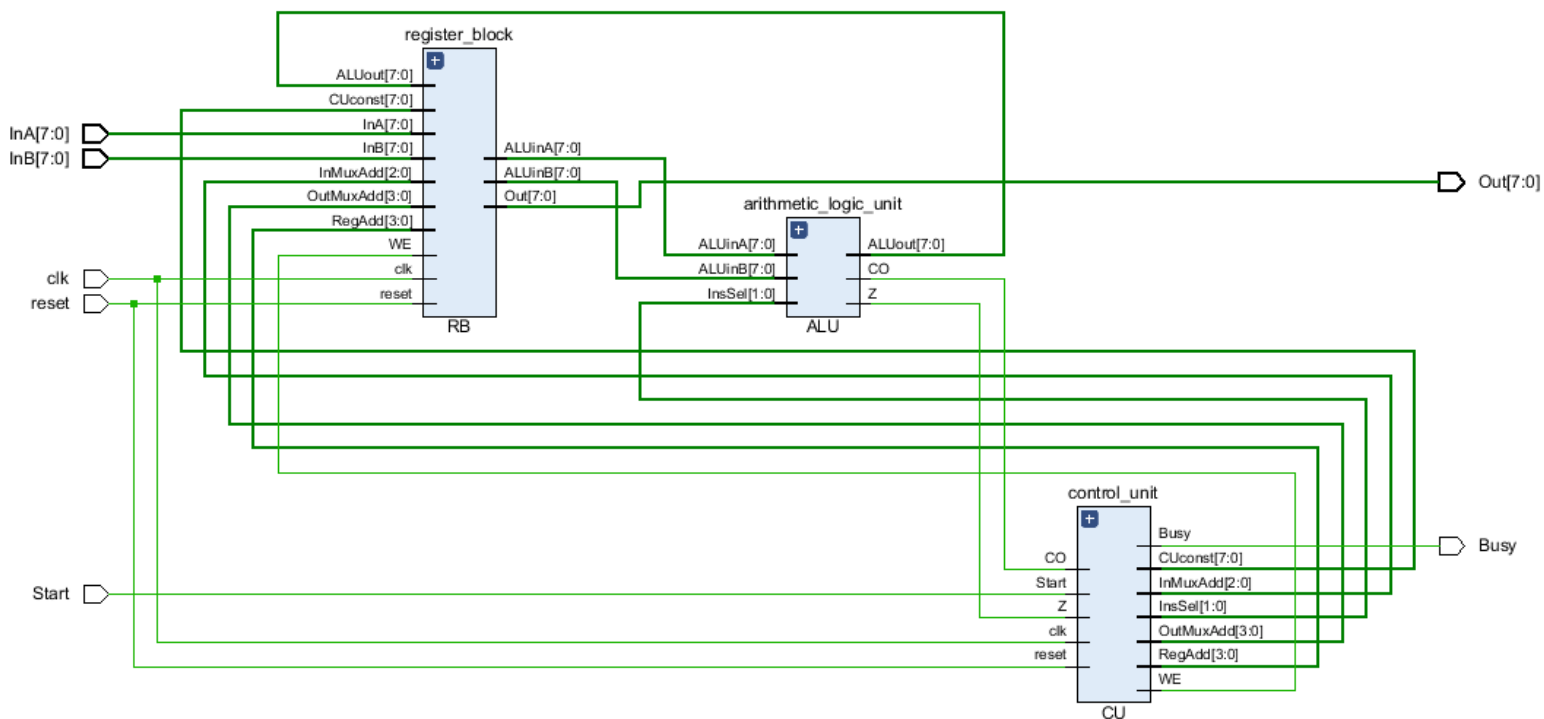


**Figure 3: RTL Schematic of the Top Module**

Name	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	F8 Muxes (15850)	Bonded IOB (210)	BUFGCTRL (32)
▼ <b>TOP</b>	315	133	24	8	28	1
> <b>arithmetic_logic_unit (ALU)</b>	67	0	0	0	0	0
<b>control_unit (CU)</b>	51	5	0	0	0	0
> <b>register_block (RB)</b>	184	128	24	8	0	0

**Figure 4: Utilization Summary**


## 4.2 ALU

In the 8-bit adder of the ALU, ripple carry adders are used.

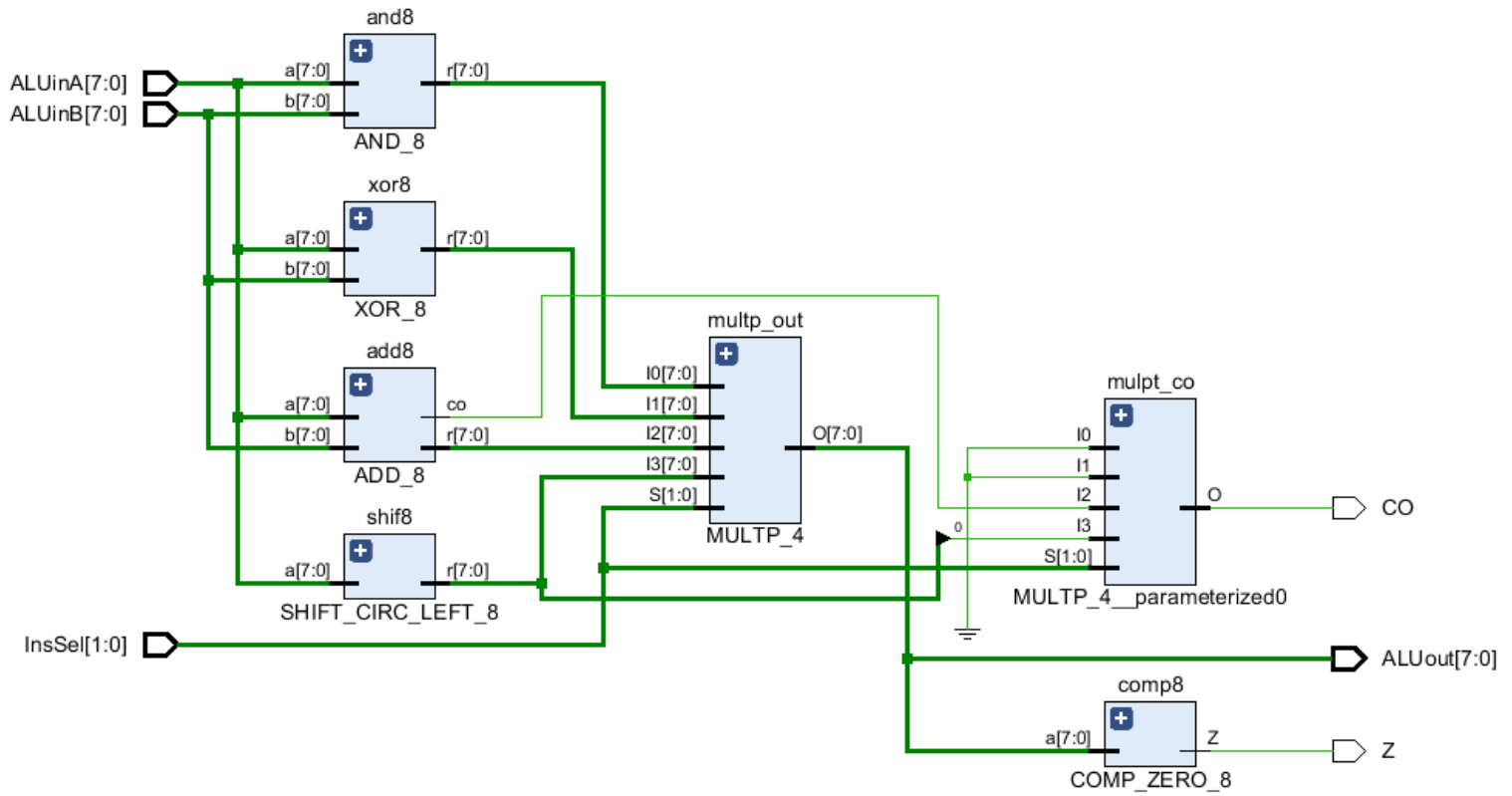


**Figure 5:** RTL Schematics of the ALU

### 4.3 Register Block

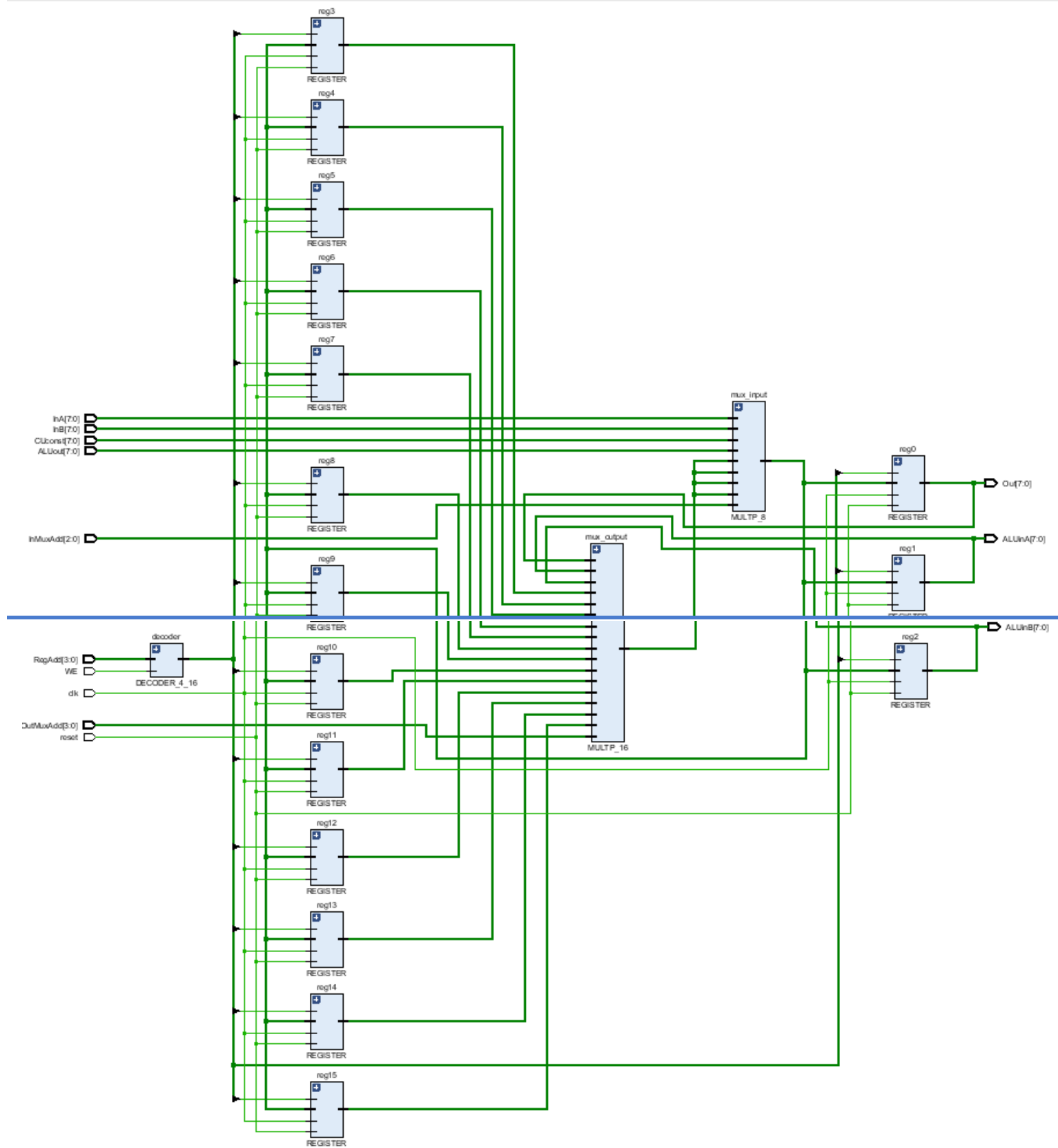

**Figure 6: RTL Schematics of the Register Block**

#### 4.4 Control Unit (CU)

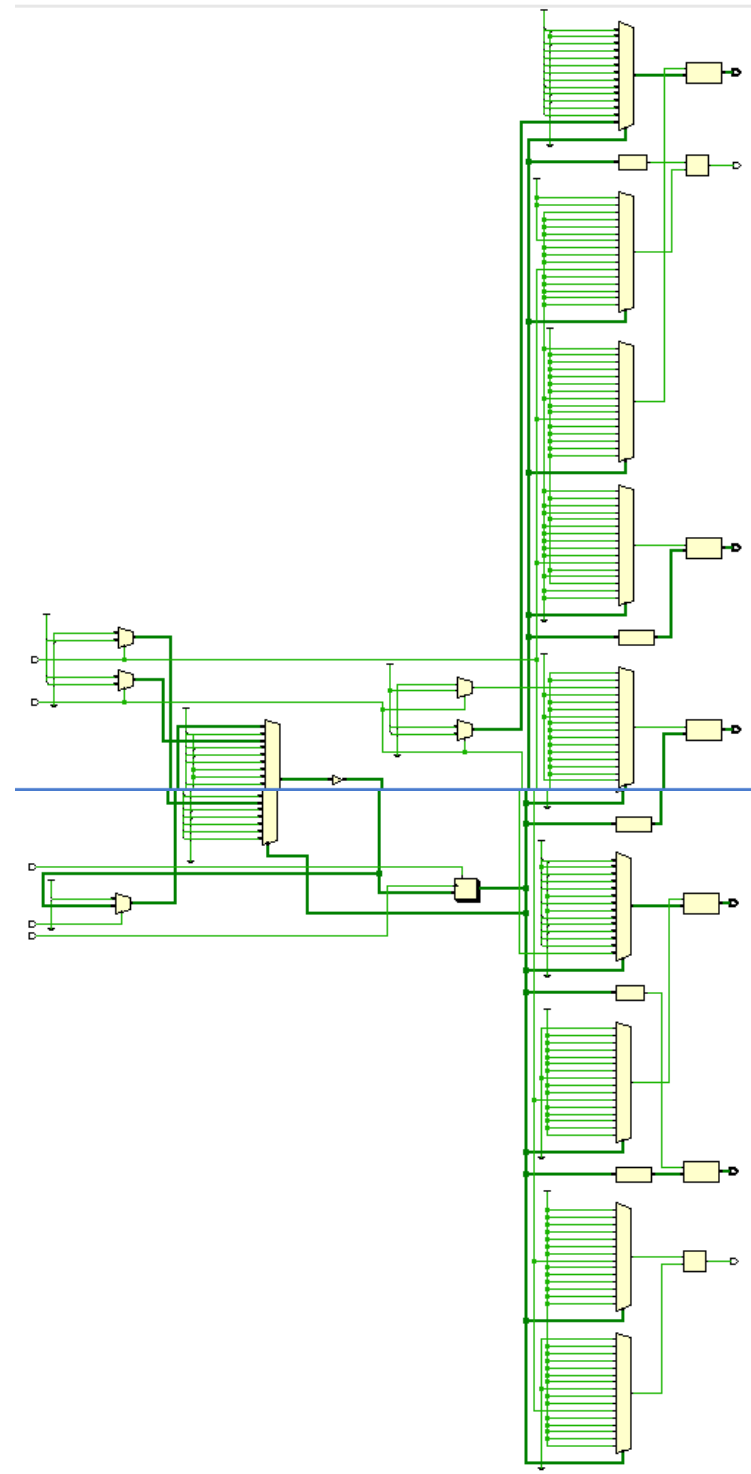


**Figure 6:** RTL Schematics of the CU



In the figure 7, random ordinary numbers,  $17/8$  is calculated.  $17/8 = 2*8 + 1$

$$0/13 = 0*13 + 0$$

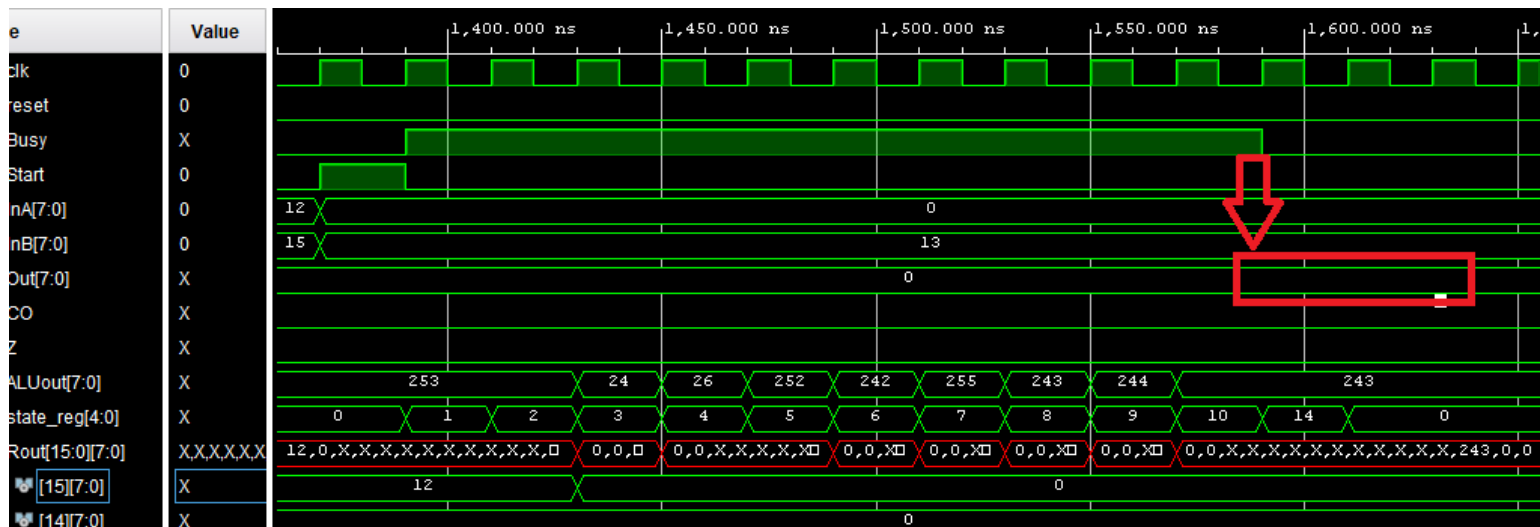


**Figure 9: Behavioral Simulation of Special Case Zero Divident**

## 5.4 The case divider is zero

Division with zero is not defined. There is no external flag as output in the design to warn user. Therefore, I chose **zero** as undefined output.

$40/0 = \mathbf{0}$  (actually undefined)

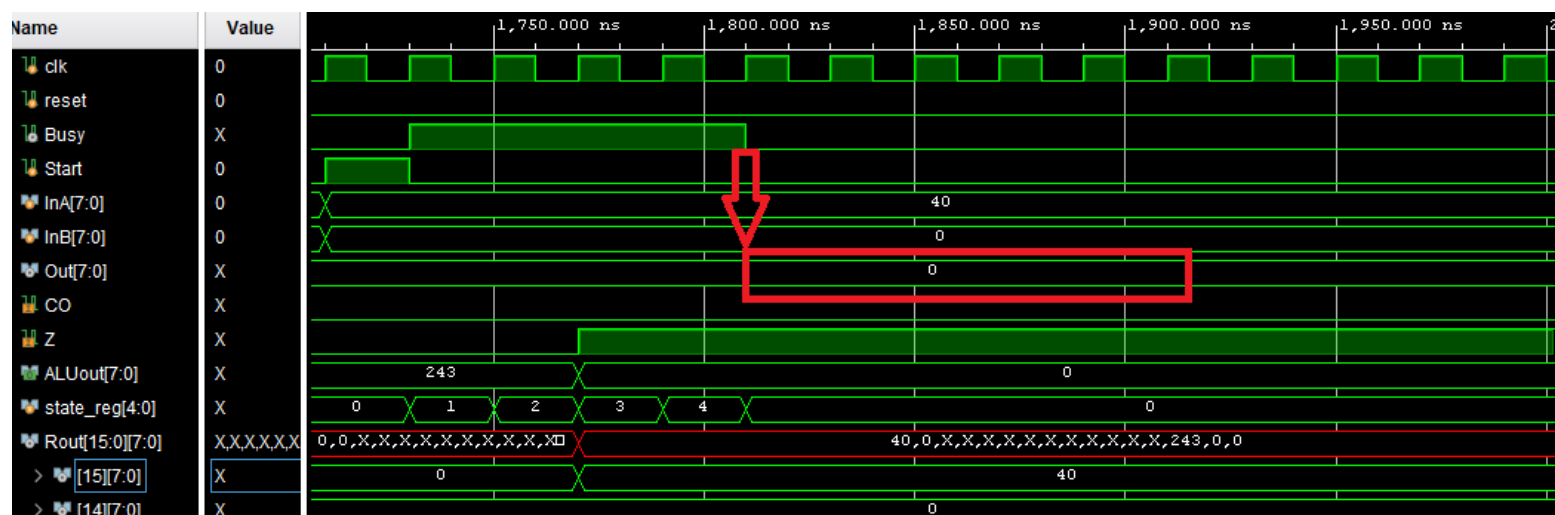

**Figure 10:** Behavioral Simulation of Special Case Zero Divider

## 5.5 The case both dividend and divider is zero

0/0 is not defined. Therefore as I did in the section 5.4, I chose zero as output.

0/0 = 0 (actually undefined)

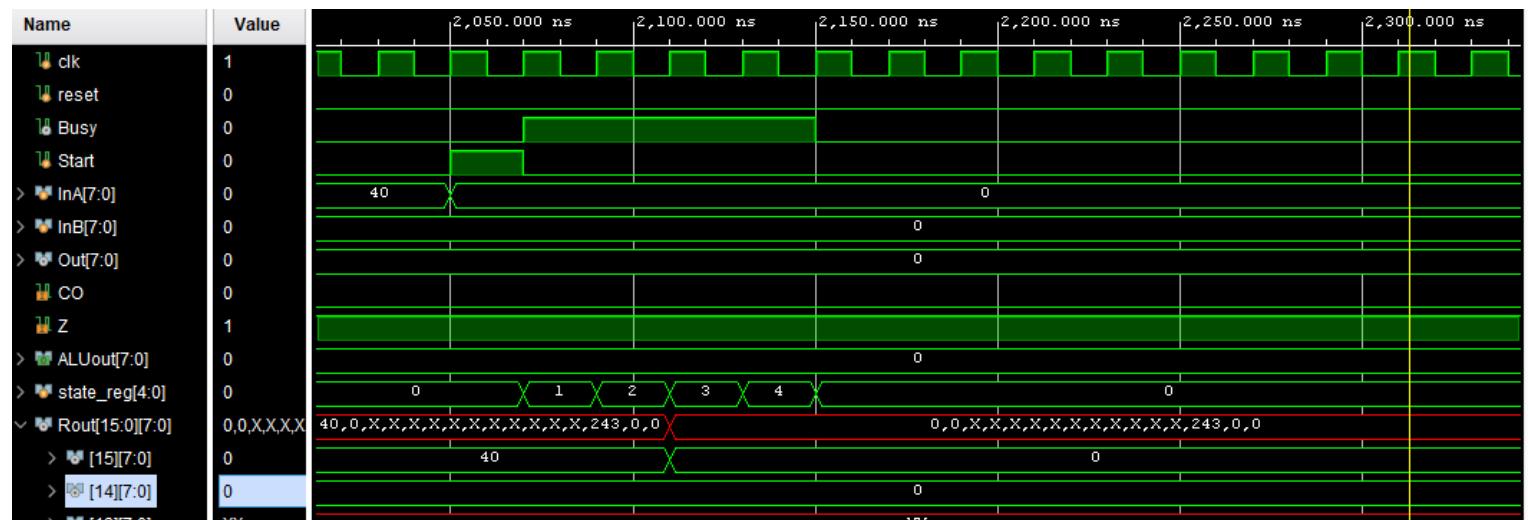


Figure 11: Behavioral Simulation of Special Case 0/0

## 5.6 Interrupted Calculation

In this section, I investigate reset signal. While a calculation is running, I sent the reset signal to stop running calculation and then I start again with different input numbers.

Firstly 213/8 calculation is given to the circuit and stopped with reset signal.

Then 13/5 calculation is done as  $2*5+3$

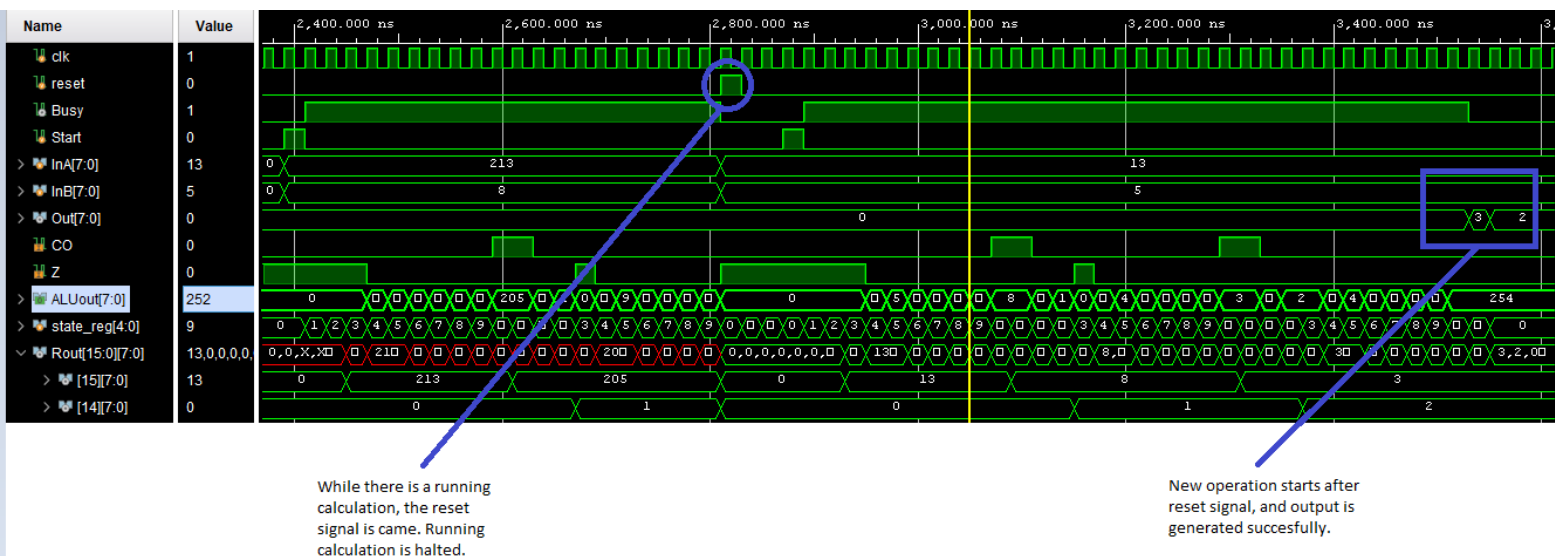


Figure 12: Behavioral Simulation of Special Case Reset Signal

**Figure 14:** Zoomed version of figure 14 to see outputs clearly.

## **6. References**

[1] “Division Algorithm”, Accessed on: Feb. 9, 2021. [Online]. Available: [https://en.wikipedia.org/wiki/Division\\_algorithm](https://en.wikipedia.org/wiki/Division_algorithm)